

Comilla University
Faculty of Engineering
Department of Computer Science and Engineering

Final Examination - 2015

Course Code: CSE 114

Course Title: Electricals Circuits and Devices

Session: 2014 - 2015

Semester: 1st Year 1st Semester


[Answer any Five of the following questions. Figures in the right-hand margin indicate full marks.]

Time: 3 Hours


Full Marks: 60

Writing anything on the question paper is strictly prohibited.

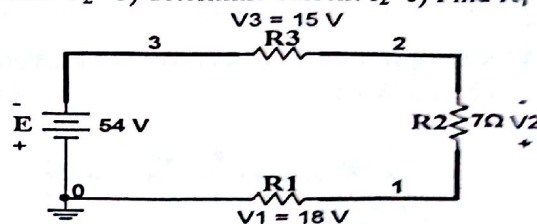
1. a. Demonstrate Kirchhoff's Voltage Law (KVL). Using KVL from the given circuit a) determine V_2 b) determine current I_2 c) Find R_1 and R_3 . 6



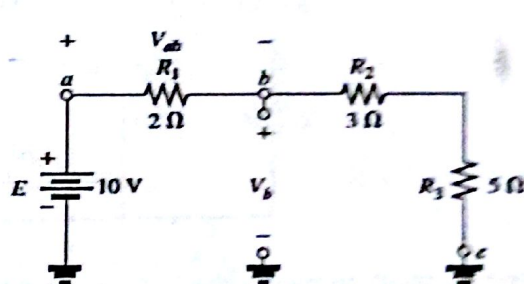
- b. If an ammeter reads 2.5 A for a period of 4 minute, determine the charge that has passed through the meter. 2
- c. How long can a 1.5 V flashlight battery provide a current of 250 mA to light the bulb if the ampere-hour rating is 16Ah? 2
- d. What is the effect of temperature on the resistance of conductor, semiconductor and insulator? 2
2. a. Define semiconductor. Classify semiconductor and give example of each type. 3
- b. State Voltage Divider Rule (VDR). For the network below: 6



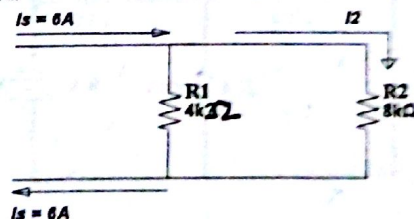
- i) Calculate V_{ab}
- ii) Determine V_b
- iii) Calculate V_c
- c. State Current Divider Rule (CDR). Determine current I_2 for the given network using CDR. 3



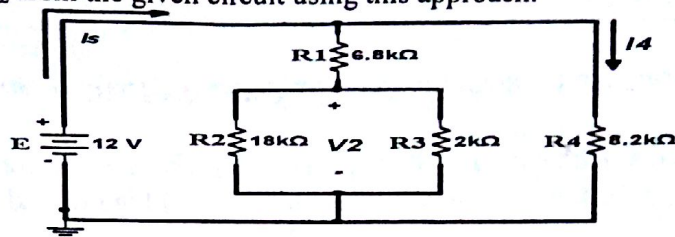3. a. Briefly explain reduce and return approach. Determine currents I_4 and voltage V_2 from the given circuit using this approach. 6




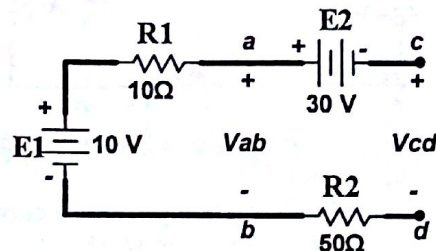- b. Briefly explain the open and short circuits. Determine voltages V_{ab} and V_{cd} for the given circuit as follows. 4




- c. Explain single subscript and double subscript notation. 2

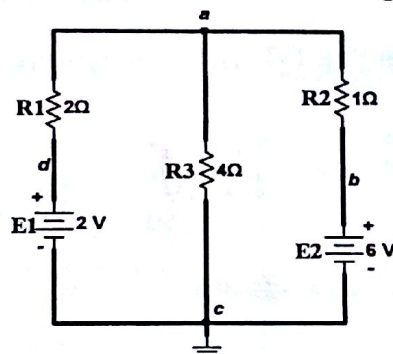
4. a. Describe the procedure of Branch-Current method. Find the magnitude and direction of the current through each resistor for the given network. 6



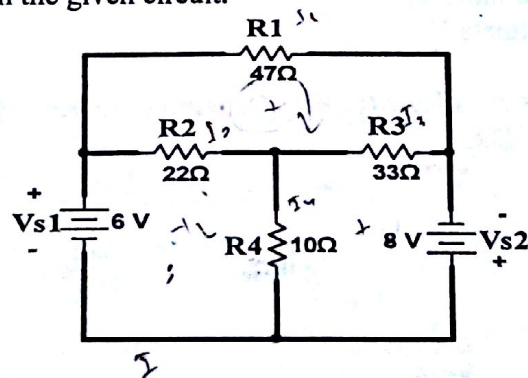
- b. Explain the mesh current method. Using the mesh current method, find the branch current in the given circuit. 6



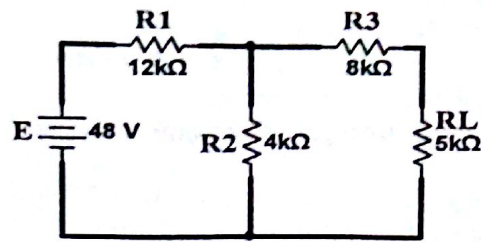
5. a. Demonstrate Thevenin's theorem. Find E_{th} , R_{th} , and load current flowing through and load voltage across the load resistor from the given circuit. 6



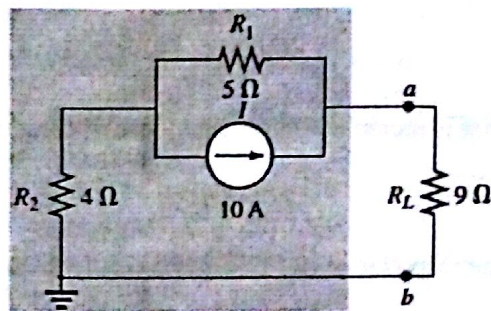- b. Find the Norton equivalent circuit for the network external to the 9Ω resistor. 6



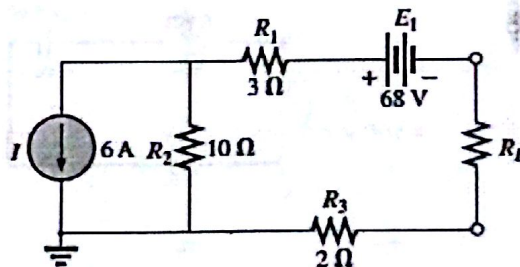6. a. Given the following network, find the value of R_L for maximum power to the load and find the maximum power to the load. 5




- b. State and explain superposition theorem with example. 4
c. What is meant by Quantity factor and Selectivity of a series resonant circuit? 3

7. a. For the following circuit:

10

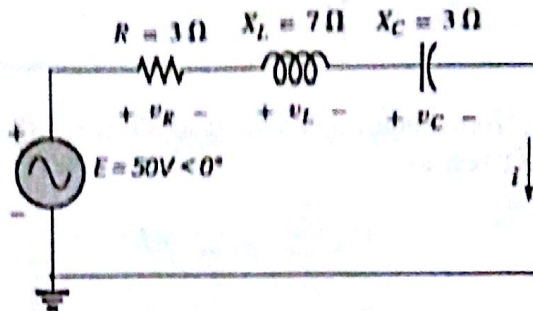- i) Calculate total impedance.
- ii) Draw the impedance diagram.
- iii) Calculate I , V_R , V_L , V_C in phasor form.
- iv) Draw the phasor diagram.
- v) Calculate total power and power factor.



b. Explain what is meant by phase and phase difference of alternating quantities.

2

8. a. Describe the response of basic R and C elements to a sinusoidal voltage or current.

6


b. The voltage across a 0.5 H coil is provided below. What is the sinusoidal expression for the current?

3

$$V = 100 \sin 20t$$

c. Using the voltage divider rule, find the voltage across each element of the circuit in the following figure.

3

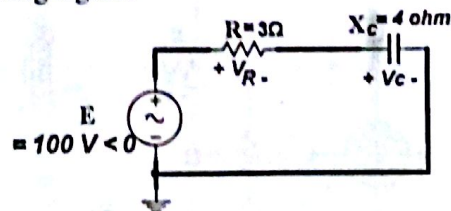

Good Luck