

**Comilla University**  
**Faculty of Engineering**  
**Department of Computer Science and Engineering**

Course Code: CSE 213  
 Session: 2013 - 2014

Final Examination - 2015  
 Course Title: Digital Logic Design  
 Semester: 2<sup>nd</sup> Year 1<sup>st</sup> Semester

[Answer any Five of the following questions. Figures in the right-hand margin indicate full marks.]

Time: 3 Hours

Full Marks: 60

Please write parts of a question serially. Writing anything on the question paper is strictly prohibited.

1. a) What is number system in computer science? Draw a block diagram of a digital computer. 3
- b) i) Performs  $101.110_2 \times 10.1_2$  ii) Performs  $101.110_2 + 10010.1_2$  4
- c) Define r's complement and (r-1)'s complement. 1
- d) Using 1's complement, Subtract M - N where N = 1000100 & M = 1010100 2
- e) Convert  $(75A1)_{16}$  to equivalent octal number. 2

2. a) Convert the BCD number 10111101 to binary. 2
- b) What is BCD? Add the BCD numbers: 10100101 + 00110011 3
- c) Determine the decimal values of the 2's complement number 10101101. 2
- d) Convert the gray code 110111010011 to binary number.. 2
- e) Subtract  $284_{16}$  from BCD. 3

- a) Obtain the weighted binary code for the base-12 digits using weights of 5421. 4

b) If  $A = \begin{array}{|c|c|c|c|} \hline 0 & 1 & 1 & 0 & 1 \\ \hline \end{array}$   
 $B = \begin{array}{|c|c|c|c|} \hline 1 & 0 & 1 & 1 & 0 \\ \hline \end{array}$

are two digital wave forms.

Find the output wave form of i)  $(A+B)'$  ii)  $B.A$  iii)  $B'+A$  iv)  $A'$

- c) Determine the odd-parity bit generated when the message consists of the ten decimal digits in the 8, 4, -2, -1 code. 4

4. a) Write the use of Karnaugh map? Use a Karnaugh map to minimize the following SOP expression : 4

$$\overline{M}\overline{N}\overline{R}\overline{S} + \overline{M}\overline{N}R\overline{S} + \overline{M}\overline{N}R\overline{S} + \overline{M}\overline{N}R\overline{S} + \overline{N}\overline{R}\overline{S} + \overline{M}\overline{N}R\overline{S} + \overline{M}\overline{N}R\overline{S} + \overline{M}\overline{N}R\overline{S}$$

- \* b) A NOR gate can function as a negative AND gate; prove it. 2.5

- c) Apply the binary numbers 1110 and 1001 to the comparator input and determine the logic level. 2.5

- d) Draw a logic diagram of a decimal to BCD encoder. 3

5. a) What is reflected code? Simplify the following expression using Boolean Algebra 1+2

$$\overline{WXY} + Z$$

- b) Draw the logic circuit for the expression  $F = A'B + B(C + D)'$  2
- \* c) Find the complement of the function  $F = x' + (y + z)(y' + z')$ . Prove that  $X + XY = X$ . 3
- d) Express the following function in sum of minterm and a product of maxterm. 4

$$F(A, B, C, D) = D(A' + B) + B'D$$

0-2-5-6-7

0-0-1-1-0-1-0-0  
0-0-1-1-0-1-0-0  
0-0-0-0-1-1-0-0  
0-0-0-0-1-1-0-0

6. a) Define Multiplexer with block diagram. 2
- \* b) Implement the following function with a multiplexer:  $F(A,B,C) = \Sigma(1,3,5,6)$  when select bit are A and B. 4
- c) Differentiate between decoder and encoder. Design a 3-to-8 line decoder. 2+4
7. a) Define shift register. Write the basic data movements in shift registers. 3
- b) Determine the timing diagram of 4-bit serial in parallel out shift register where the register initially contains all 1's. 4
- c) Show the steps when 1011 being entered into the serial in serial out shift register. 3
- d) How shift register is used as a keyboard encoder? 2
8. a) Differentiate between combinational circuit and sequential circuit with block diagram. 3
- b) Define flip-flop. Explain the clocked RS flip-flop with necessary diagram. 6
- c) What do you mean by binary counter? Why asynchronous counter is referred to as ripple counter? 3

Good Luck !