

Comilla University
Faculty of Engineering
Department of Computer Science and Engineering
2nd Year 1st Semester Final Examination - 2020
Course Code: CSE 2105 Session: 2018 - 2019
Course Title: Digital Logic Design

[Answer any Five of the following questions. Figures in the right-hand margin indicate full marks.]

Time: 3 Hours

Full Marks: 60

Writing anything on the question paper is strictly prohibited.

- ✓ 1 a) What is meant by the base of a number system? Explain principle of Duality. 1+2
9 b) Which of the codes are called invalid codes in BCD and why? 3
c) Why is Gray code not suitable for arithmetic operations? Explain with example. 4
d) Convert the binary code 101101 to Gray code. 2
- ✓ 2 a) Distinguish between a Half-Adder and a Full-Adder. 2
b) Implement a Full-Adder using two Half-Adders and an External OR gate. 3
c) Construct a 16-bit Parallel Binary Adder using 4-bit Parallel Binary Adder ICs. 3
7 d) Represent the decimal number -27 as an 8-bit number in i) sign-magnitude representation, 4
ii) 1's complement representation, and iii) 2's complement representation.
- ✓ 3 a) Differentiate between Combinational circuit and Sequential Circuit. 3
b) Design a combinational logic circuit that controls the passage of a signal A according to the 6
following requirement:
i) Output Y will equal A when control inputs B and C are same. ✓
ii) Y will remain HIGH when B and C are different.
- ✓ 4 c) Implement the following function using only NAND gates: 3
$$f(A, B, C) = A\bar{B} + \bar{A}B + C$$
- 4 a) Minimize the following function using k-map and realize using NOR gates only 5
 $\Pi M(1, 2, 3, 8, 9, 10, 11, 14). d(6, 7, 15)$
b) Design a 2-bit magnitude comparator circuit. 4
c) What are the difference between a ripple carry adder and a look-ahead carry adder? 3
- ✓ 5 a) Using binary arithmetic evaluate the binary arithmetic expression: 2
$$101110 + 110111$$

b) The binary ripple-carry addition algorithm used in (a), can be implemented using a one-bit full adder that takes two input bits a and b and a carry-in bits c and compute a sum bit z and a carry-out bit d. The diagram below illustrates the input and outputs of a one-bit adder.
i Draw a truth table for the one-bit full adder. 2
ii Based on the truth table obtained in (i) write the logical expressions for the sum bit z and carry-out bit d. 4

iii. Simplify the logical expressions obtained in (ii), and draw one circuit diagram for one-bit full adder.

 


Fig. 1

- 6 ✓ a) Design a 16:1 multiplexer using 4:1 multiplexer ICs. Mention some applications of multiplexers.
- 10 ✓ b) Implement a full adder logic circuit using multiplexers.
- 10 ✓ c) Design a 1-to-8-line Demultiplexer.
- 8 ✓ a) What is the difference between a Latch and a Flip-Flop?
- 12 ✓ b) Design an S-R latch using two 2-input NAND gates.
- 12 ✓ c) How can Race-Around Condition be eliminated with necessary diagram
- 12 ✓ d) Draw the logic diagram with truth table of a clocked D-type Flip-Flop.

① diff ~~to~~ → shift regi and counter

② explain → siso shift regia operate